

**Science Practice Exam  
Chapters 5 and 14 ANSWERS**

- |      |       |       |
|------|-------|-------|
| 1. A | 6. A  | 11. C |
| 2. B | 7. A  | 12. C |
| 3. D | 8. D  | 13. A |
| 4. C | 9. A  | 14. B |
| 5. B | 10. B | 15. B |

16.  $V = 12 \text{ v}$                        $R = 4 \Omega$                        $I = ?$

$$I = \frac{V}{R}$$

$$I = \frac{12 \text{ v}}{4 \Omega}$$

$$I = 3 \text{ amps}$$

**The current intensity is 3 amps.**

17.



18.  $E = 900 \text{ kJ} \times 1000 = 900\,000 \text{ J}$   
 $t = 45 \text{ minutes} \times 60 = 2700 \text{ seconds}$   
 $P = ?$

$$P = \frac{E}{t}$$

$$P = \frac{900\,000 \text{ J}}{2700 \text{ s}}$$

$$P = 333.33 \text{ watts}$$

**The electrical power of this appliance is 333.33 watts.**

19. Conventional current flows from positive to negative.

20.  $P = 2000 \text{ W} \div 1000 = 2 \text{ kW}$   
 $t = 4 \text{ hours}$   
 $E = ?$

$$E = P \cdot t$$

$$E = 2 \text{ kW} \cdot 4 \text{ h}$$

$$E = 8 \text{ kW} \cdot \text{h}$$

**The energy used is 8 kW·h**

21. When a glass rod and silk are rubbed together, electrons travel from the glass rod to the silk. The glass has lost electrons giving it a positive charge and the silk has gained electrons (from the glass) leaving the silk with a negative charge.

22.  $I = 300 \text{ mA} \div 1000 = 0.3 \text{ A}$

$$R = 100 \Omega$$

$$V = ?$$

$$V = I \cdot R$$

$$V = 0.3 \text{ A} \cdot 100 \Omega$$

$$V = 30 \text{ volts}$$

**The voltage of the power supply is 30 volts.**

23.  $P = 250 \text{ w}$

$$t = 30 \text{ mins} \times 60 = 1800 \text{ seconds.}$$

$$E = ?$$

$$E = P \cdot t$$

$$E = 250 \text{ w} \cdot 1800 \text{ s}$$

$$E = 450\,000 \text{ J}$$

$$E = 450\,000 \text{ J} \div 1000$$

$$E = 450 \text{ kJ} \times 30 \text{ days} = 13\,500 \text{ kJ}$$

**13 500 kJ of energy will be consumed in one month.**

24.  $R = 50 \Omega$

$$V = 120 \text{ V}$$

$$P = ?$$

$$I = \frac{V}{R}$$

$$I = \frac{120 \text{ v}}{50 \Omega}$$

$$I = 2.4 \text{ amps}$$

$$P = V \cdot I \quad P = 120 \text{ v} \cdot 2.4 \text{ A} \quad P = 288 \text{ watts}$$

**The power is 288 watts.**

25. A)  $V = 220 \text{ v}$        $R = 30 \Omega$

$$T = 15 \text{ mins or } 900 \text{ seconds or } 0.25 \text{ hours}$$

$$I = \frac{V}{R}$$

$$I = \frac{220 \text{ v}}{30 \Omega}$$

$$I = 7.33 \text{ amps}$$

$$P = V \cdot I \quad P = 220 \text{ v} \cdot 7.33 \text{ A} \quad P = 1612.6 \text{ w}$$

$$E = P \cdot t \quad E = 1612.6 \text{ w} \times 900 \text{ s} \quad E = 1\,451\,340 \text{ J}$$

**The coffee maker used 1 451 340 J of energy.**

b)  $E = P \cdot t$

$$E = 1.6126 \text{ kW} \cdot 0.25 \text{ h}$$

$$E = 0.40315 \text{ kW} \cdot \text{h} \times \$0.05 = 0.02$$

$$0.02 \times 365 \text{ days} = 7.30$$

**It would cost \$7.30 to run the coffee maker for a year.**