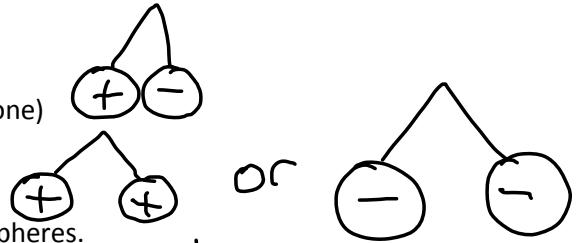


Chapter 5 Questions


Name: _____

Electrical Charges


1. Opposite charges attract / ~~repel~~ each other. (circle one)
2. Like charges ~~attract~~ / repel each other. (circle one)



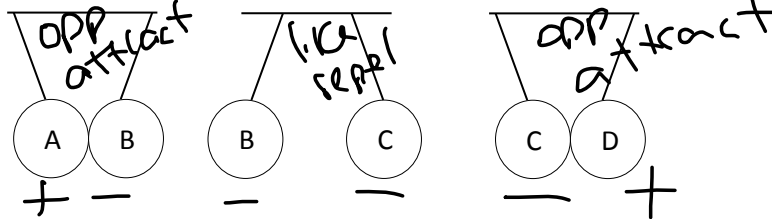
3. The following experiment is set up using charged spheres.



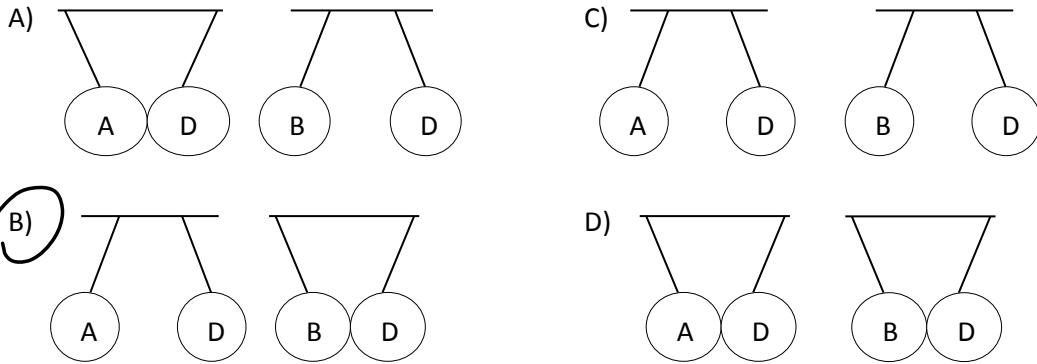Spheres A and D are then set up side by side, as well as spheres B & D. Which diagram below correctly shows what would happen?



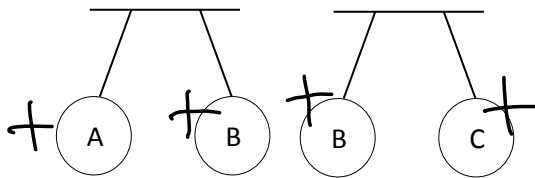4. If A is positively charged, what is the charge of C? positive



5. Based on the electrostatic series, (found on the next page) if silk is rubbed on a glass rod - which one is gaining electrons?

Silk would gain electrons, and get a negative charge

6. What would happen if you used a cotton cloth to wipe your glass window clean?
 - A) The glass window would become negatively charged
 - B) The cotton cloth would become negatively charged
 - C) The cotton cloth would become positively charged
 - D) The glass window & cotton cloth would stay neutrally charged

Electrostatic Series	
TENDENCY	SUBSTANCE
Acquire a Negative Charge	Rubber
	Ebonite
	Polyethylene (Plastic)
	Cotton
	Silk
	Wool
	Glass
Acquire a Positive Charge	Acetate
	Fur

Memorize units!

Ohm's Law, Electrical Power & Energy Consumed Questions

1. What units are used for the following variables?

I – Current Intensity amps (A)

V – Potential Difference volts (v)

R – Resistance ohms (Ω)

P – Electrical Power watts or kilowatts

E – Electrical Energy joules or w/h or kW/h

T – time secs (when E is joules) or hours (when E is in w/h or kW/h)

2. A 6kW appliance is turned on for 20 minutes, how much energy (in watt-hour) did it use?

$$P = 6 \text{ kW} \xrightarrow{\times 1000} 6000 \text{ W}$$

$$t = 20 \text{ mins} \xrightarrow{\div 60} 0.33 \text{ h}$$

$$E = ? \text{ w/h}$$

$$E = P \cdot t$$

$$= 6000 \text{ W} \cdot 0.33 \text{ h}$$

$$= 1980 \text{ w/h}$$

3. A circuit consists of a 21 V battery connected across a single resistor. If the current in the circuit is 3 A, calculate the size of the resistor (calculate the resistance).

$$V = 21 \text{ V}$$

$$I = 3 \text{ A}$$

$$R = ? \Omega$$

$$R = \frac{V}{I} \quad R = \frac{21 \text{ V}}{3 \text{ A}} \quad R = 7 \Omega$$

4. A 20-volt relay has a coil resistance of 200 ohms. How much current does it draw?

$$V = 20 \text{ V}$$

$$R = 200 \Omega$$

$$I = ? \text{ A}$$

$$I = \frac{V}{R} \quad I = \frac{20 \text{ V}}{200 \Omega} \quad I = 0.1 \text{ A}$$

5. A 500W appliance is turned on for 180 minutes. How much energy in watt-hour was used by the appliance?

$$P = 500 \text{ w}$$

$$t = 180 \text{ mins} \xrightarrow{\div 60} 3 \text{ h}$$

$$E = ? \text{ w/h}$$

$$E = P \cdot t$$

$$= 500 \text{ w} \cdot 3 \text{ h}$$

$$= 1500 \text{ w/h}$$

6. A transformer is connected to 120 volts. Find the current if the resistance is 480-ohms

$$V = 120 \text{ v}$$

$$R = 480 \Omega$$

$$I = ? \text{ A}$$

$$I = \frac{V}{R}$$

$$I = \frac{120 \text{ v}}{480 \Omega}$$

$$I = 0.25 \text{ A}$$

7. The price of electricity in Quebec is approximately \$0.07 per kW·h. A student turns on a 60 watt light bulb for 7 hours every day for 30 days. What will be the monthly electric bill for the light bulb?

$$P = 60 \text{ w} \xrightarrow{\div 1000} 0.06 \text{ kW}$$

$$t = 7 \text{ h}$$

$$\text{for 30 days} > 210 \text{ h}$$

$$E = P \cdot t$$

$$= 0.06 \text{ kW} \cdot 210 \text{ h}$$

$$= 12.6 \text{ kW/h}$$

$$\text{Cost}$$

$$\times 12.6 \text{ kW/h}$$

$$\times 0.07$$

$$= 0.88$$

Circuits


1. What are the three elements a circuit needs for it to work?

• power supply (battery)

• resistance (light bulb, resistor)

• Wires

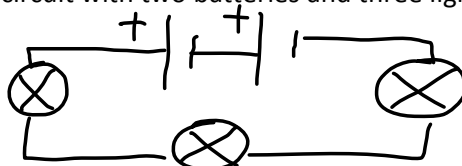
2. Draw a series circuit with two batteries and three light bulbs.



3. Draw a parallel circuit with one battery and three light bulbs.



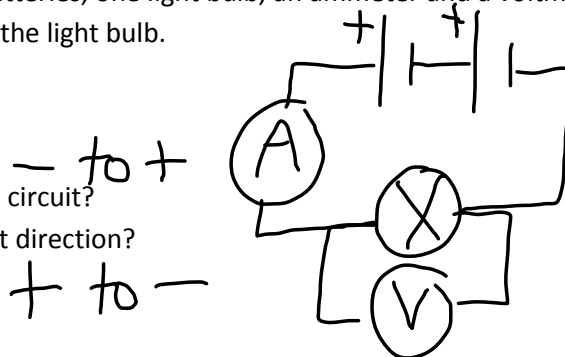4. Draw a circuit that includes two batteries, one light bulb, an ammeter and a voltmeter finding the potential difference of the light bulb.




5. Which way do electrons travel in a circuit?

6. Which way is conventional current direction?

7. State whether the motor will work in the circuit below in the following situations:

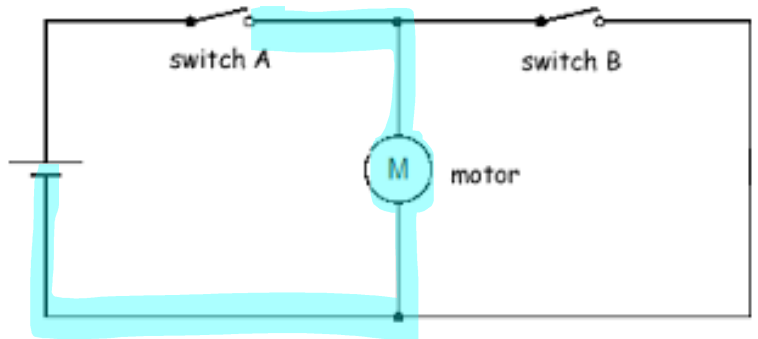- a) Switch A is on, Switch B is off, the motor is working
- b) Switch A is on, Switch B is on, the motor is working
- c) Switch A is off, Switch B is off, the motor is not working
- d) Switch A is off, Switch B is on, the motor is not working




8. Which bulbs will turn on if switch A is closed and switch B is open?

None!



9. Which bulbs will turn on if switch A is open and switch B is closed?

Bulb Y & X

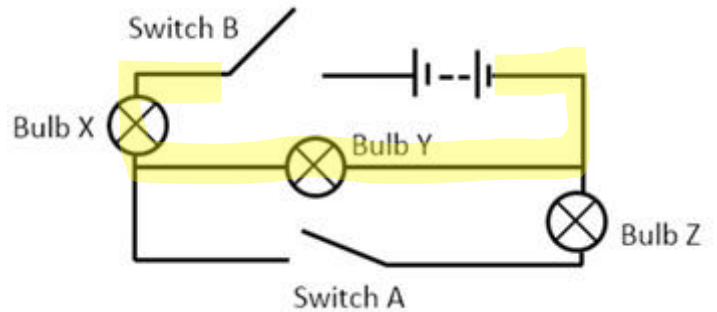


Magnets

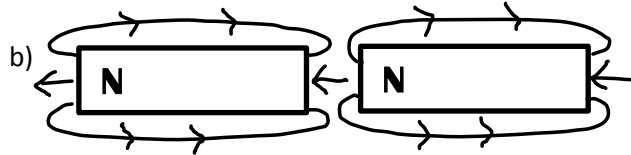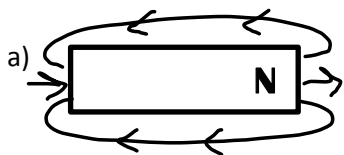1. Like poles attract (~~repel~~) each other & Opposite poles attract (~~repel~~) each other.
2. Each magnet has 2 poles, a north pole and a south pole.
3. Draw the magnetic field lines of the following:




4. Where would the compass' be pointing if placed in the following locations near the magnets?


a)

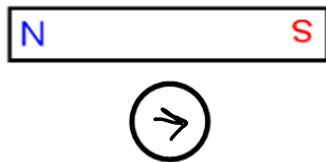

b)

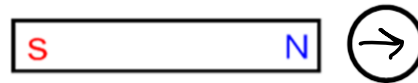

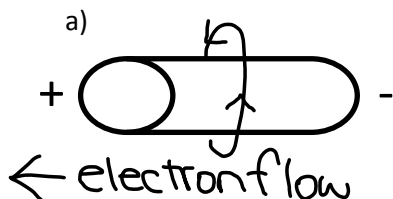5. Which way is the current flowing on the following?



b)

